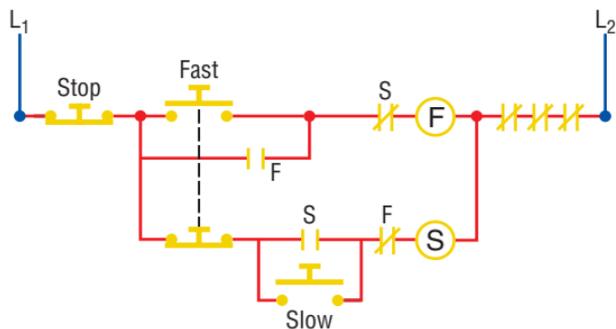




TWO-SPEED STARTING



Note this circuit's interlocks:

- Closing the fast switch also opens the Slow leg of the circuit.
- When the S coil is activated, it opens the normally closed S contact in the Fast leg of the circuit.
- When the F coil is activated, it opens the normally closed F contact in the Slow leg of the circuit.